



# KIET Group of Institutions, Ghaziabad, U.P.

Department of Applied Science










## Fundamentals of Electronics Engineering (BEC201)

### Assignment 1 (Unit 1)

Name of Faculty: Dr. Manish Kumar Singh

Sem –II

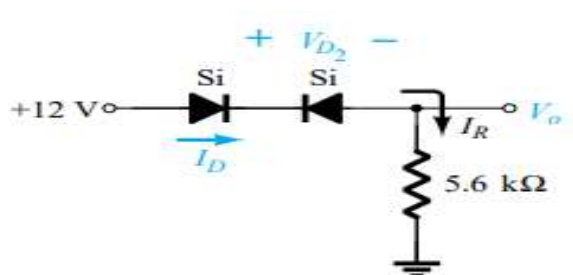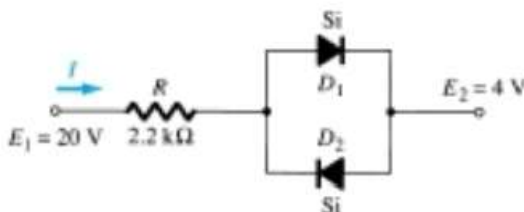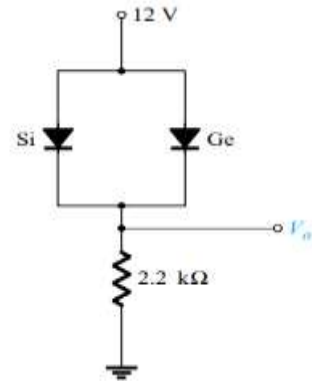S.N.	Questions	BL
1	Draw and explain the diode equivalent model of Si diode, Ge diode and ideal diode.	3
2	Define clipper. Explain different types of clipper.	2
3	Determine $I_D$ , $V_{D2}$ , and $V_o$ for the circuit 	3
4	Determine the current $I$ for the network 	4
5	Determine the voltage $V_o$ for the network 	3
6	Determine the output waveform for the circuit of given figure:	4

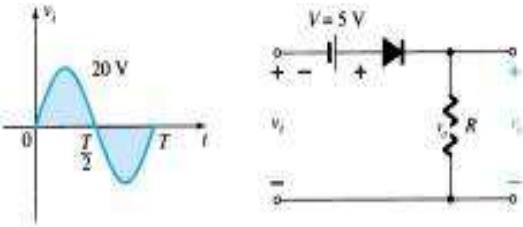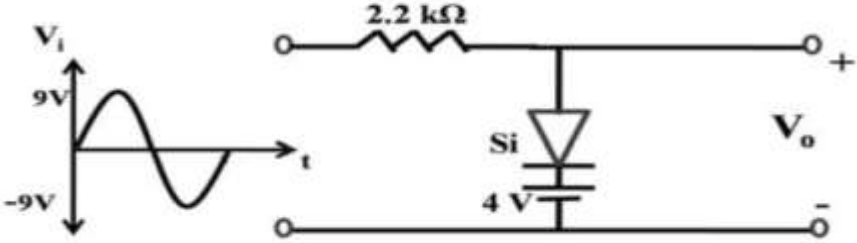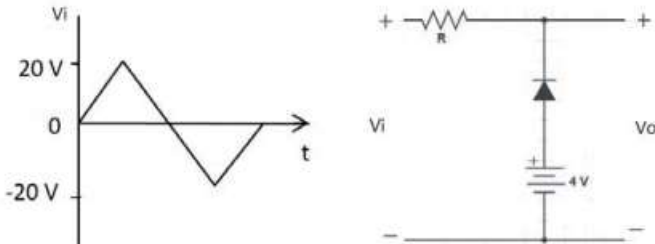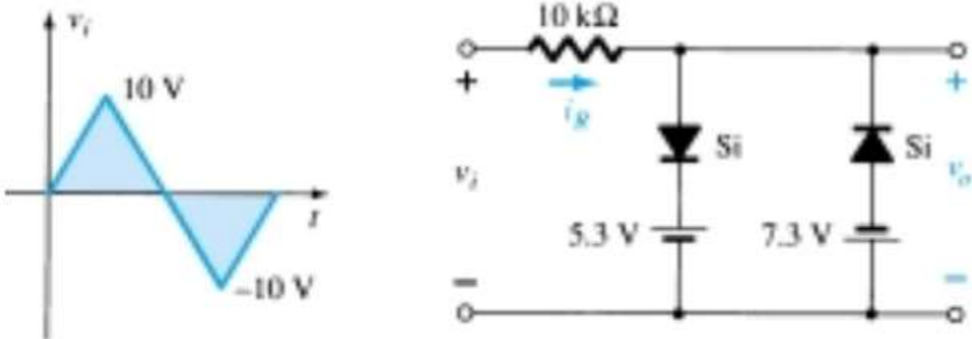		
7	<p>Determine and draw output voltage for given network.</p> 	5
8	<p>Determine the output waveform for the following circuit</p> 	5
9	<p>Analyse and draw the Output waveform (<math>V_o</math>) of the network given in fig .</p> 	4
10	<p>Define clamper. Explain different types of clamper.</p>	2

